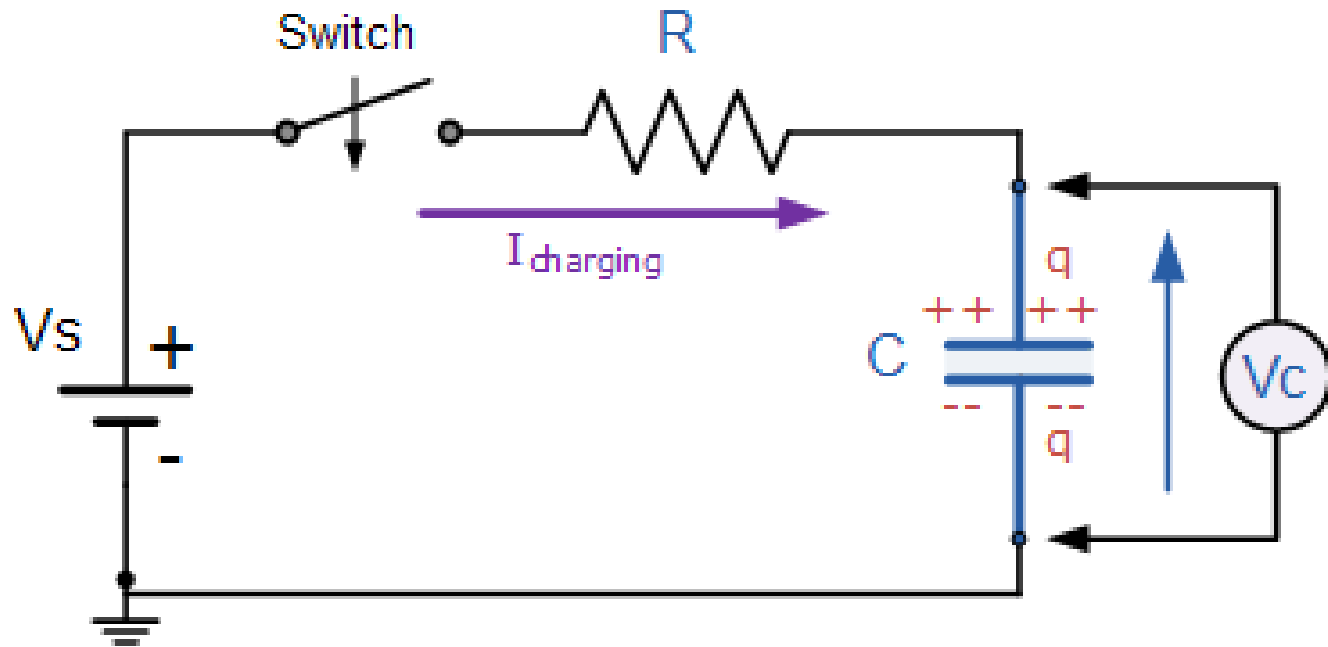


Measurements Lab

RC time constant

NC State University

Basic RC circuit



Consider a capacitor initially charged to V_0 , and connected to a resistor Kirchoff Voltage Law (Loop Law): $V_r + V_c = 0$ or $V_r = -V_c$

The same current runs through each element: $i_r = i_c$.

Using voltage laws for the capacitor and resistor give us

$$V_c = 1/C q_c$$

$$V_r = R i_r$$

and the relation between charge and current, $q_c' = i_c$, together with the voltage and current relations, we can obtain a differential equation of motion

$$q_c' = - (1/RC) q_c$$

To see it in terms of current, take its time derivative:

$$i_c' = - (1/RC) i_c$$

Or in terms of voltage, using

$$V_c' = - (1/RC) V_c$$

All of these equations of motion have an easy solution, e.g.



$$V_c = V_0 e^{-t/RC}$$

Charging time response

$$\tau = RC$$

$$V_{charge}(t) = V_0(1 - e^{-t/\tau})$$

$$V_{discharge}(t) = V_0e^{-t/\tau}$$

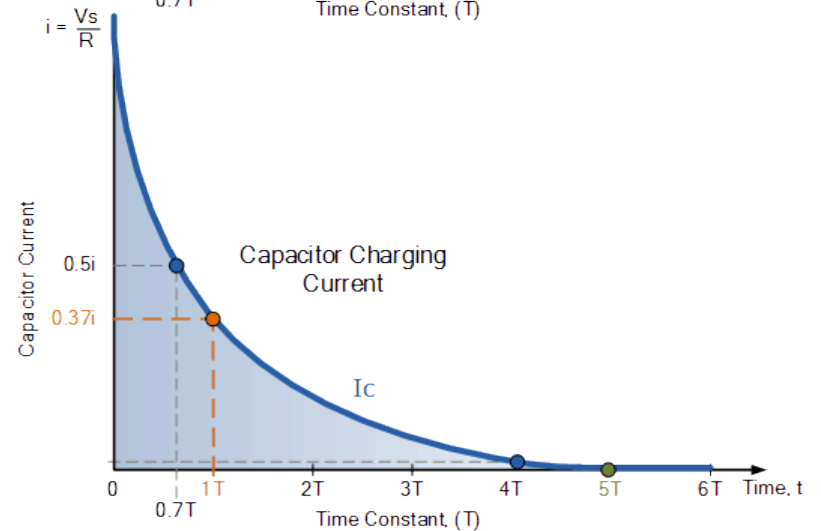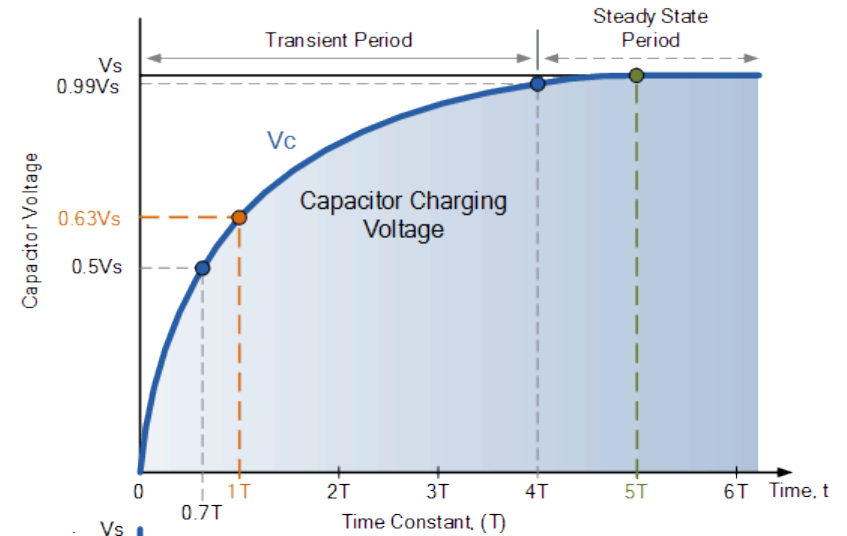

Inverting operational amplifier

The principle of operation is that the voltage difference at the + and – inputs will be maintained at zero and no current flows into the input terminals. If the + input is grounded then the – input must satisfy $V = 0$. The currents through the two resistors must be equal and opposite. Ohm's law gives:

$$\frac{V_{out}}{V_{in}} = \frac{-iR_f}{iR_{in}}$$

The minus sign on the output voltage gives rise to the name “inverting”. The gain in signal is:

$$Gain = \frac{R_f}{R_{in}}$$

